

Practical Concerns and Solutions in Integrated High-Resolution ADCs

揭路

清华大学



High Resolution ADC Needs

- **General specifications**
 - **High SNDR:** $>90\text{dB}$
 - **High efficiency:** $>175\text{dB}$ FoMs
 - **Med-low speed:** kHz $\sim$ MHz BW



IoT Devices



Sensor Readout




Biomedical



Acoustic

Varieties of Solutions Exist

 
- **General specifications**
 - **High SNDR:** >90dB
 - **High efficiency:** >175dB FoMs
 - **Med-low speed:** kHz ~ MHz BW



 Problem Solved?

- High **SNDR** and **FoM** – Achieved
- Higher **BW** – on the way
- But we concern **MORE** in practice!
 - Especially for integrated ADC IP

E.g. Wearable devices, IoT, smart sensing...





Process and Area Concerns

- Many **advanced** high-resolution **ADCs** are made in **old process**
 - And they are large too
- But SoC prefers **advanced process**



Published high-resolution ADCs

[B. Murmann, "ADC Survey" Jun 2021]

  



Driving Effort

  - Driving high-resolution Nyquist ADC is a big challenge
 - C_s is large for low KT/C
- Oversampling does not fully relax driving effort
 - Need to charge C_s faster



Nyquist And Single-End Capability

  - Many applications need a “Nyquist” ADC
 - Support **single-shot conversion**
 - Support **multiplexing**
- Single-ended capability is also desired
 - Compatible with **various input formats**
 - i.e., a high full-scale CMRR



And More ...

- **Decoupling**

- Many high-resolution ADCs heavily rely on **large decaps**
- Typically for stabilizing / denoise references
- E.g. SAR ADC

- **Calibration and trimming**

- Foreground calibration / trimming increases **testing cost**
- Background calibration / DEM increases **P/A cost**

- **PVT robustness**

- Sometimes ignored by academic designs

...

The Complete Wish List

- High SNDR and FoM —————→ ✓ Lots of solutions

Practical Features:

- Advanced process compatible —————→ ✗ OTA, high swing -> more digital?
- Low area —————→ ✗ SAR / pipe -> oversampling?
- Easy driving —————→ ✗ SAR / pipe -> oversampling?
- Nyquist capable —————→ ✗ SAR / pipe -> oversampling?
- Single-ended capable —————→ ✗ SAR / pipe -> oversampling?
- Easy decoupling —————→ ✗ DSM -> Incremental?
- Calibration / trimming free —————→ ✗ CT-DSM ?
- PVT Robust —————→ ✗ Open loop based ?

...


The Complete Wish List

- ✓ High SNDR and FoM

Practical Features:

- ✓ Advanced process compatible
- ✓ Low area
- ✓ Easy driving
- ✓ Nyquist capable
- ✓ Single-ended capable
- ✓ Easy decoupling
- ✓ Calibration free
- ✓ PVT Robust


...

 

The “Zoom” Framework


- **Slow coarse stage + single-bit DSM**

 - ✓ Effectively multi-bit
- ✓ Inherent linear DSM
- ✓ Low DAC toggle rate
- ✓ Small input to LF
- ✗ DAC mismatch unsolved
- ✗ Only works for DC
- ✗ Massive SC input sampling




Mismatch Error in DAC

 - Mismatch error in DAC brings nonlinearity




The “Real Time”(RT) DEM

 - Circulate the elements **step-by-step** for a **complete round**



 
$\text{Error} \propto D_{IN} \Rightarrow \text{Distortion}$



$\text{Error} \propto D_{IN} \Rightarrow \text{Linear gain error}$

The “Real Time”(RT) DEM

 - ✓ Remove mismatch **completely**
- ✓ Simple implementation




RT-DEM DAC

E4				E4		E4	E4	E4	
E3			E3		E3	E3	E3		
E2		E2			E2	E2		E2	E2
E1	E1				E1		E1	E1	E1
...									
4	1				3				2
...	$1 \cdot (E1 + E2 + E3 + E4) / 4$				$3 \cdot (E1 + E2 + E3 + E4) / 4$				...

$\text{Error} \propto D_{IN} \implies \text{Linear gain error}$


The “Real Time”(RT) DEM

 - ✓ Remove mismatch **completely**
 - ✓ Simple implementation
 - Limitations
 - High OSR
 - 1st-order IDSM
- } OK for advanced process




Decoupled Stages with RT-DEM

 - ✓ Simple hardware
- ✓ Completely remove mismatch
- ✓ Low toggle rate
- ✓ Code independent ripple
- ? Cannot track AC



Introduce Tracking Mechanism

 - ✓ Simple hardware
- ✓ Completely remove mismatch
- ✓ Low toggle rate
- ✓ Code independent ripple
- ✓ Tracks input
- ✓ Gain calibration free




Implement Coarse ADC

- ✓ Simple hardware
- ✓ Completely remove mismatch
- ✓ Low toggle rate
- ✓ Code independent ripple
- ✓ Tracks input
- ✓ Gain calibration free


? Needs complicated B2T

 - What is the **simplest ADC** providing “thermometer” output?




Simplest – Counting ADC

 - Ramp DAC's output till V_{IN}
- Count the steps of ramping
- ✓ Reusing the DEM and DAC
 - ✓ No B2T!
 - ✓ Low power
 - ✓ Compact



Even Simpler – Comparator Reuse

 - Ramp DAC's output till V_{IN}
- Count the steps of ramping
- ✓ Reusing **all** hardware
 - ✓ No B2T!
 - ✓ Low power
 - ✓ Even more compact!




Switch to Continuous-Time

- **Gm-C loop filter (integrator)**

- ✓ Fast, settling free
- ✓ High efficiency
- ✓ Linearity relaxed by small input
- ✓ Low swing - scaling friendly


- **Cap-coupled input**

- ✓ Easy driven
- ✓ kT/C noise free

 


“Zoom of Incremental + Counting” (ZIC)

 - ✓ High SNDR
- ✓ Good scalability
- ✓ Small and simple
- ✓ Easy driving
- ✓ Stable Vref ripple
- ✓ Nyquist capable
- ✓ Calibration free
- ✓ PVT Robust




Input Network Concern

 - Cap coupling – easy driving
- ✗ Cannot accept DC input




$$C_U = 12.5\text{fF}$$
$$C_{IN} = 132C_U$$

Input Network Concern

 


- Cap coupling – easy driving
- Reset during idle
 - ✓ Reset to $V_{IN,CM}$ gives great CMRR
 - ✗ Induce kT/C noise

Input Network Concern

 


- Cap coupling – easy driving
- Reset during idle
- Apply **chopping** – kT/C is DC error
 - ✓ Also suppress **flicker noise** and **leakages**

Input Network Concern

 



- Cap coupling – easy driving
 - Reset during idle
 - Apply chopping
- $V_{IN,CM} = (V_{IN}^+ + V_{IN}^-)/2$
- Sample both V_{IN} on split C_{IN}
 - **Chopping** is embedded

Full Schematic

 

Dynamic Power Concern

  Only two DFFs are flipping
at each DEM step



Circular
Shift
Register

FIR

7x DFF

FIR

Minimum size
comparator

Divider chain


CNT_{DSM}

CNT_{Track}

- ✓ Small gate count → ~100uW @ 500M F_{CLK}
- ✓ Can be further reduced in advanced process

Clock Generation Concern




 
- The 500MHz clock sounds costly to generate? - Not really
 - ✓ Loose jitter requirement: 3ps rms for 105dB
 - ✓ Loose frequency precision: even $\pm 20\%$ F_{CLK} is tolerable
- A “crappy” free-running relaxation oscillator* is enough
 - $\sim 200\mu\text{W}$ @ 500M (post sim)
 - $10 \times 40\mu\text{m}$
 - No trimming needed



*Not used in actual measurement



Prototype ADC

- 28nm CMOS
- Core Area: 90x160 μm^2

   
 


Single-Tone Test @20kS/s




2^{16} -FFT, 16x Averaged

  

CMRR and Single-Ended Input

  

PVT Measurements

   

SOTA Design Comparison

	ISSCC'22 This work		VLSI'20 E. Elan	VLSI'18 B. Wang	ISSCC'21 S. Mondal	ISSCC'22 J. Steensgaard	ISSCC'20 J. Liu
Architecture	Zoom (Cnt' + CT-IDSM)		Zoom (SAR + DT-DSM)	DT-IDSM	CT-DSM	Multi-step SAR	NS-SAR
Process (nm)	28		160	65	65	180	40
Area (mm ²)	0.014		0.27	0.134	0.39	0.78	0.061
Supply (V)	0.9 / 1.2		1.8	1.2	1.2	1.8 / 5	1.1
OSR	2¹⁴	2¹³	87.5	256	150	1	25
F _{s,nyq} (kS/s)	20	50	40	40	48	2000	80
Power (mW)	0.47	0.59	0.44	0.55	0.14	8.5	0.067
SNDR (dB)	102.9	100.1	106.5	100.8	100.9	105.3	90.5
FOM _S (dB)	176.2	176.4	183.1	176.4	183.3	186.0	178.2



Includes decimation filter

Practical Features

	ISSCC'22 This work	VLSI'20 E. Elan	VLSI'18 B. Wang	ISSCC'21 S. Mondal	ISSCC'22 J. Steensgaard	ISSCC'20 J. Liu
Architecture	Zoom (Cnt' + CT-IDSM)	Zoom (SAR + DT-DSM)	DT-IDSM	CT-DSM	Multi-step SAR	NS-SAR
Full-Scale CMRR @ DC	>100dB	>100dB	Not Support	Not Support	140dB	Not Support
Multiplexing / Single-Shot	Incremental	Not Support	Incremental	Not Support	Nyquist Sampling	Not Support
PVT	Stable	Stable	Stable	Not Report	Stable	Stable
Mismatch Solution	RT-DEM	DWA	DWA	1bit-DAC	Cal. + DEM	MES
Reference Ripple	Code Independent	Code Dependent	Code Dependent	Negligible (RDAC)	Code Dependent	Code Dependent
Input Network	Cap Coupling	Switched Cap	Switched Cap	Resistive	Switched Cap	Switched Cap

Area & Process Highlight

[B. Murmann, "ADC Survey" Jun 2021]

  

Conclusion

- **Prototype Highlights:**
 - Smallest for 90+dB SNDR
 - Highest SNDR for 28nm
 - Nyquist and single-end capability
- **Suggestions for designing integrated high-resolution ADC**
 - Always consider the deployment in practice
 - Take advantage of fast digital (e.g. high OSR)
 - Simple analog circuitry is preferred
 - Architecture hybridization is promising

Thanks!

Q&A